

Electrical Design

Project A

Design a Buck-Boost Convertor. To learn about buck-boost convertor, look at the videos in the link below. Buck Convertor starts from the 15th video.

<https://www.youtube.com/playlist?list=PLmK1EnKxphikP6c9Yc9kGYO0kvrBEOwN8>

To Do:

1. Design a schematic and upload it on the canvas.
2. After the schematic review, design the pcb and upload it on canvas.

P.S. Watch all the videos as they will be very helpful in general

You may use either Altium or Eagle/KiCAD.

Project B

Design a filter for Transcranial Magnetic Stimulation – Electrocorticography experiments (TMS- ECoG)

To design this low-pass anti-aliasing filter, use the following specification:

- cut-off frequency: 500Hz
- Gain: -80 dB/dec

You may use Op-amps/instrumentation amps and passive components to design this circuit.

Ensure that the filter can be bypassed upon a stimulation trigger. (Else you end up with ringing artifact due to the impulse response of the filter)

Input channels: Channel 1 and Reference Channel (From raw electrode signal)

Output channels: Filtered Channel 1 and Reference Channel (To main ECoG amplifier)

(You can make it for 4 channels sharing the same reference channel if you have time)

Potential application: <https://www.ncbi.nlm.nih.gov/pmc/articles/PMC3499764/>

To Do:

Design the filter topology

(great series of videos here:

Filtering 101: <https://www.youtube.com/playlist?list=PL64A193CF0B94C5D3>

Sallen-Key 101:

<https://www.youtube.com/watch?v=DEV7l66D6Ys&list=PLiwaj4qabLWxp1kilM2Pa6H-db8zygpNo>

Design a pcb for the filter – Use either Eagle/KiCAD or Altium